
X-Over Diagram for Celestion (Ditton) 66 Studio Monitor

Circuit split for Tri Wiring

Updated 22/02/2015

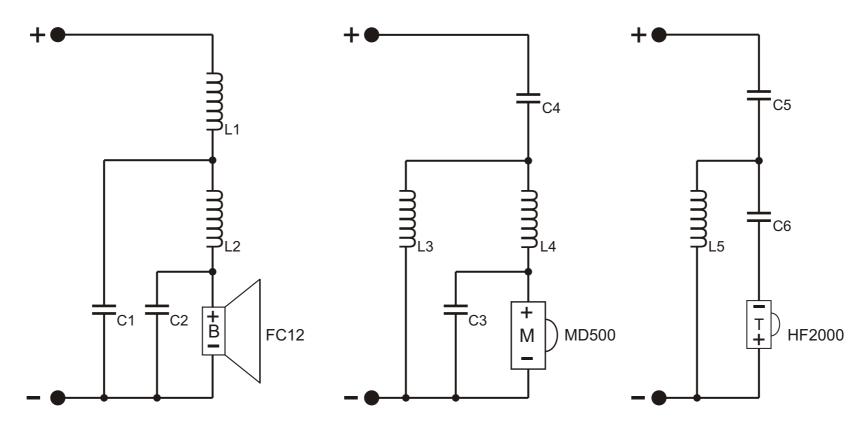

Copyright J K Wynn © 22/02/2015 Not for commercial reproduction

PARTS LIST

Nominal values used with no adjustment for driver ageing/performance loss etc.

Based on results I have had from experimenting and not on rumers or theory as to what should work.

Drivers/components are for later "Woodies" using MD500 mid range, which after trying both types
I prefer over the MF500, as it integrates better, especially noticeable at higher volumes.

FC 12 Bass #T.1600 MD500 Mid Range #T.2618 HF2000 Tweeter type #T.2373.

Note: Replacing electrolytics with Polypropylene caps and ESR simulating resistors does not work in this circuit and the resulting sound when used is truly awful.

Caps should be replaced like for like, that is, film caps for the tweeter and electrolytics for all others.

Part brands are what I used and are by no means definitive, electrolytics are Mundorf ECap (Plain) 70v Bipolar and Alcap 100v Bipolar, Polypropylene Film Caps are Ansar Supersound.

Coils are standard issue.


See Diagram on page 1

C_1	70f	Alcon
C1	72uf	Alcap
C2	72uf	Alcap
C3	4uf	Alcap
C4	24uf	Parallel 22uf ECap + 1uf ECap + 1uf Ansar PP*
C5	4uf	Ansar PP
C6	6.2uf	Parallel 4.7uf + 1.5uf Ansar PP's
L1	3.5 mH	
L2	2.2 mH	
L3	2.2 mH	
L4	0.34 mH	
L5	0.14 mH	

*Note: The addition of a 1uf PP cap in the 24uf mix adds a bit of body to the mid range without the draw backs associated with using a total value made of PP's, do not use more than 5% PP here.

If the Seas 19TFF1 tweeter is to be used the following changes should be made:
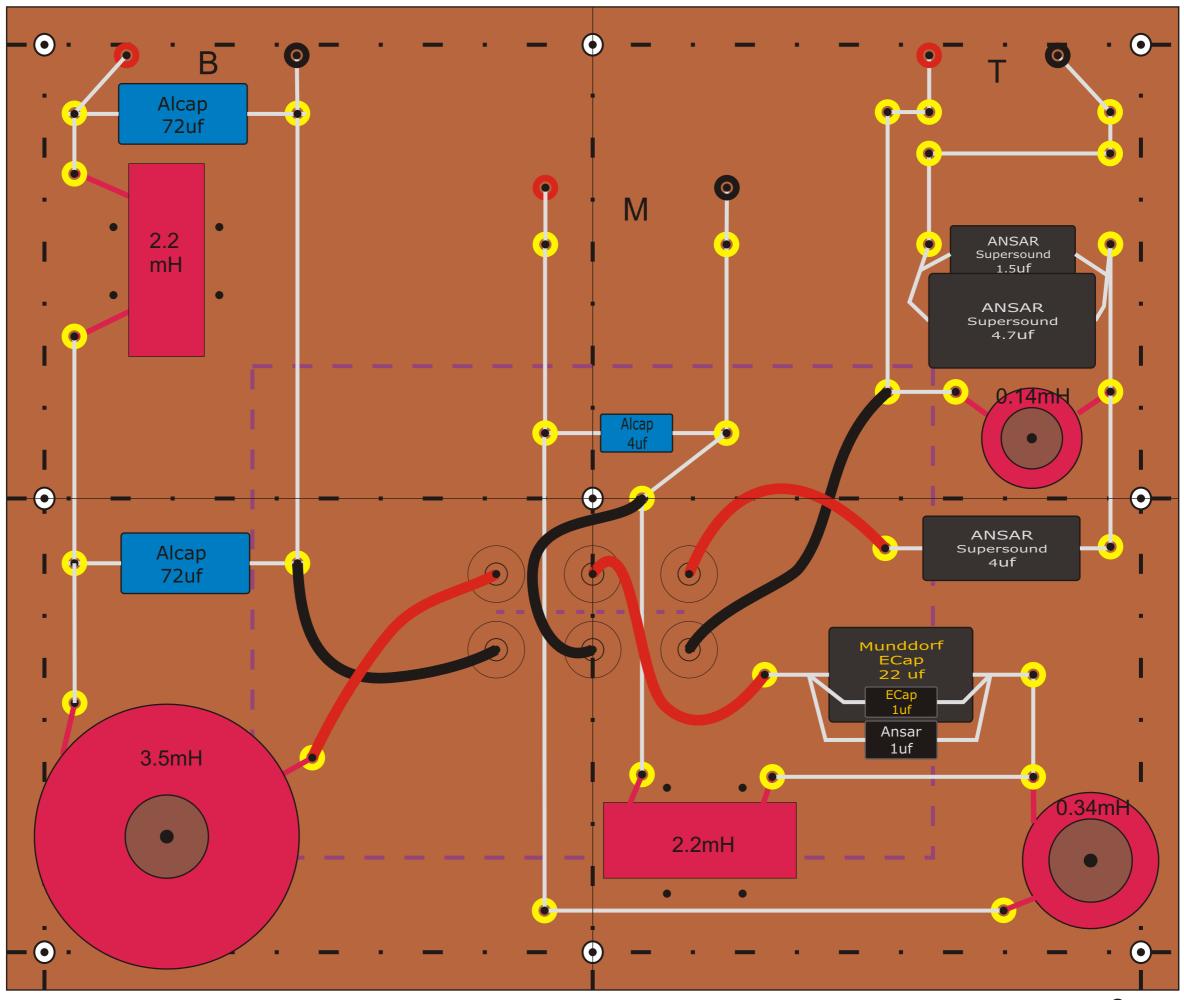
```
C5 3.3uf Ansar PP
C6 9uf Ansar PP
L5 0.17mH Jantzen air core with a DCR of around 0.15 to 0.2 Ohm.
```



Stock coils are used but spacing is improved to avoid interaction, the board is 310 x 260 mm. This the largest that will fit through the driver aperture and it is located behind the ABR unit away from the large magnet on the Bass driver.